

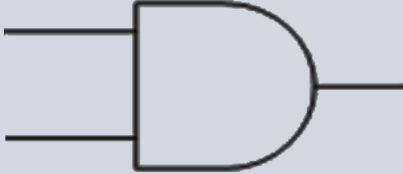

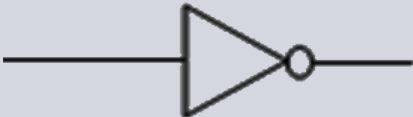
LOGIC CIRCUITS

Individual homework – Cîrstea Andrei
Daniel

THEORY ASPECTS







Basic Gates

Gate	Symbol
AND	
OR	
NOT	

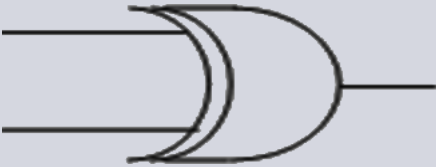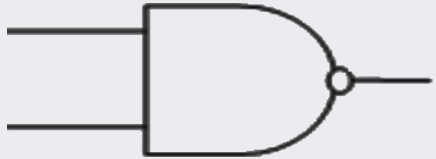

Derived Gates

Gate	Symbol	Boolean Function
XOR		$A \oplus B = \bar{A}B \vee A\bar{B}$
NAND		$A \uparrow B = \overline{AB} = \bar{A} \vee \bar{B}$
NOR		$A \downarrow B = \overline{A \vee B} = \bar{A} \bar{B}$
NXOR		$A \otimes B = \overline{AB} \vee AB$ $= (\bar{A} \vee B)(\bar{B} \vee A)$



Solution




Problem statement

Exercise 3.

Draw a logic circuit having 3 input wires and containing all basic and derived gates. Write the corresponding Boolean function, simplify it and then draw a simplified circuit equivalent to the initial one.



Chosen Circuit

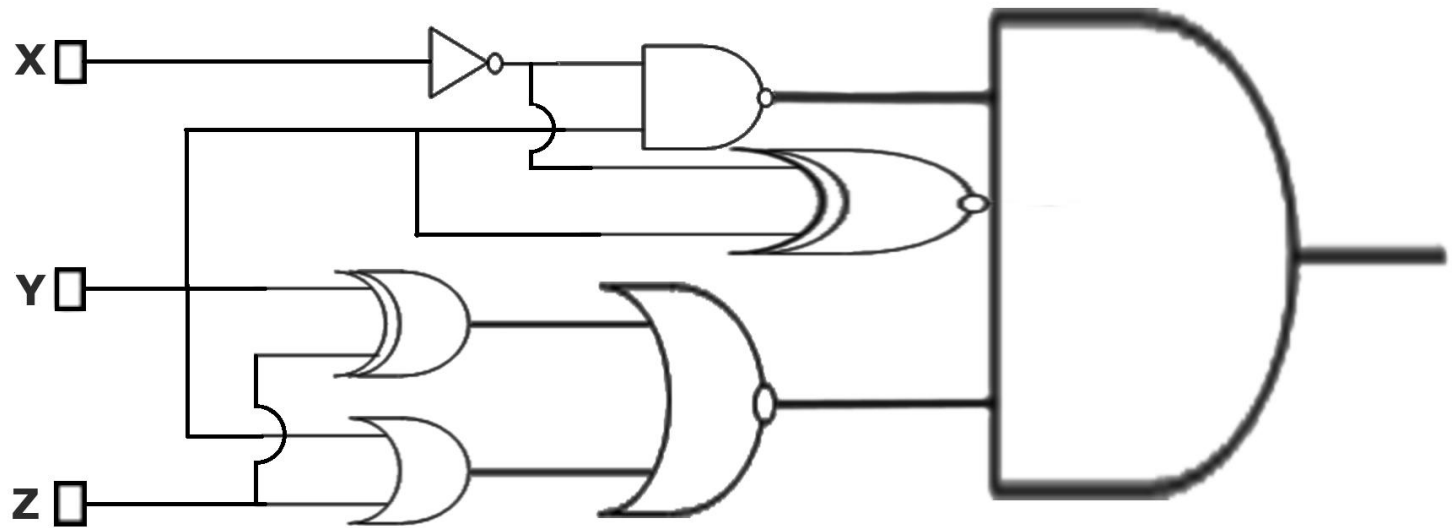

Corresponding Boolean formula

$$f(x, y, z) = (\bar{x} \uparrow y) \wedge (\bar{x} \otimes y) \wedge [(y \oplus z) \downarrow (y \vee z)]$$



Simplification

$$\begin{aligned} f(x, y, z) &= (\bar{x} \uparrow y) \wedge (\bar{x} \otimes y) \wedge [(y \oplus z) \downarrow (y \vee z)] = \\ &= (x \vee \bar{y}) \wedge (\bar{x} \vee \bar{y}) \wedge (x \vee y) \wedge [((\bar{y} \wedge z) \vee (y \wedge \bar{z})) \downarrow (y \vee z)] \\ &= (x \vee \bar{y}) \wedge (\bar{x} \vee \bar{y}) \wedge (x \vee y) \wedge (y \vee \bar{z}) \wedge (\bar{y} \vee z) \wedge \bar{y} \wedge \bar{z} \\ &= (\text{absorption laws for } \bar{y} \text{ and } \bar{z}) = \\ &= (x \vee y) \wedge \bar{y} \wedge \bar{z} = (x \vee y) \wedge (\bar{y} \wedge \bar{z}) = (x \wedge \bar{y} \wedge \bar{z}) \vee (y \wedge \bar{y} \wedge \bar{z}) \text{ (the last} \\ &\text{parenthesis is always false because of } y \wedge \neg y) \\ &= x \wedge \bar{y} \wedge \bar{z} \end{aligned}$$

$$\text{So, } f(x, y, z) = x \wedge \bar{y} \wedge \bar{z}$$



Simplified circuit

